

1522/204

1602/204

**MICROELECTRONICS, ELECTRICAL
PRINCIPLES II, INSTRUMENTS AND
ELECTRONIC FAULT DIAGNOSIS**

June/July 2023

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONIC TECHNOLOGY
(TELECOMMUNICATION OPTION)**

MODULE II

**MICROELECTRONICS, ELECTRICAL PRINCIPLES II, INSTRUMENTS AND ELECTRONIC
FAULT DIAGNOSIS**

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator;

Mathematical tables;

Intel 8080/8085 instruction set;

Drawing instruments.

*This paper consists of **EIGHT** questions in **THREE** sections; **A, B** and **C**.*

*Answer **ONE** question from section **A**, **TWO** questions from section **B** and **TWO** questions from section **C** in the answers booklet provided.*

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

*Candidates should answer the questions in **English**.*

This paper consists of 9 printed pages.

**Candidates should check the question paper to ascertain that all
the pages are printed as indicated and that no questions are missing.**

SECTION A: MICROELECTRONICS

Answer **ONE** question from this section.

1. (a) (i) Distinguish between software and hardware with respect to microprocessor systems.

(ii) Describe each of the following buses in a microprocessor:

I. control bus;

II. data bus.

(6 marks)

(b) State **four** features of the pentium microprocessor family.

(4 marks)

(c) **Figure 1** shows the pin diagram of the 8085 microprocessor IC.

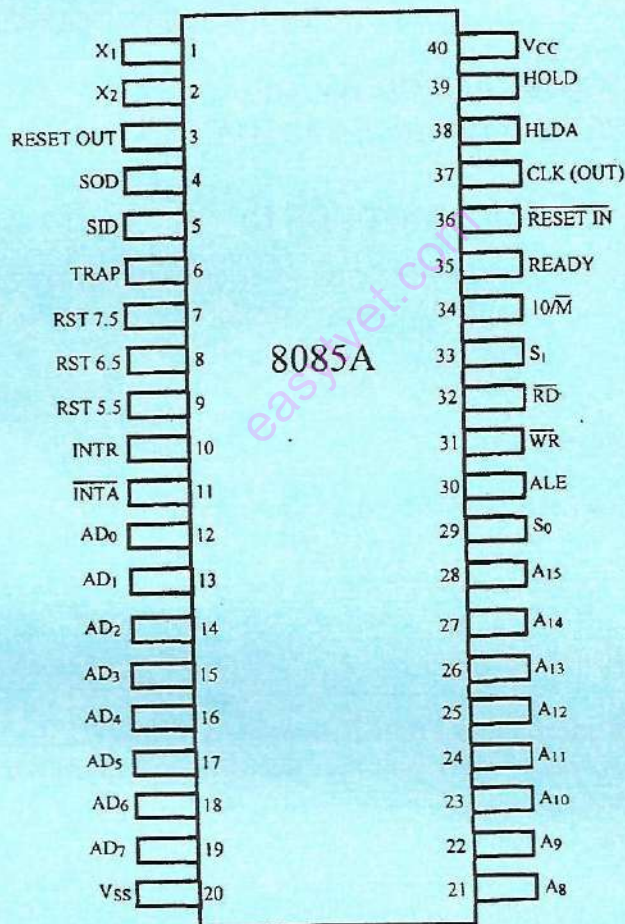


Fig. 1

(i) Explain the function of each of the following pins:

- I. 32
- II. 34
- III. 3
- IV. 5

(ii) Identify the pins for each of the following:

- I. power supply;
- II. data bus.

(10 marks)

2. (a) Define each of the following with respect to memories:

- (i) volatile;
- (ii) random access;
- (iii) address.

(6 marks)

(b) Draw a schematic block diagram to show how a $64\text{K} \times 8$ PROM can be realised from two $32\text{K} \times 8$ PROM chips. (9 marks)

(c) Write an assembly language program to add 16 H to 34 H and save the result in register D. (5 marks)

SECTION B: ELECTRICAL PRINCIPLES II

Answer TWO questions from this section.

3. (a) (i) State two advantages of digital-over analogue - instruments.
- (ii) Figure 2 shows a block diagram of a digital voltmeter.

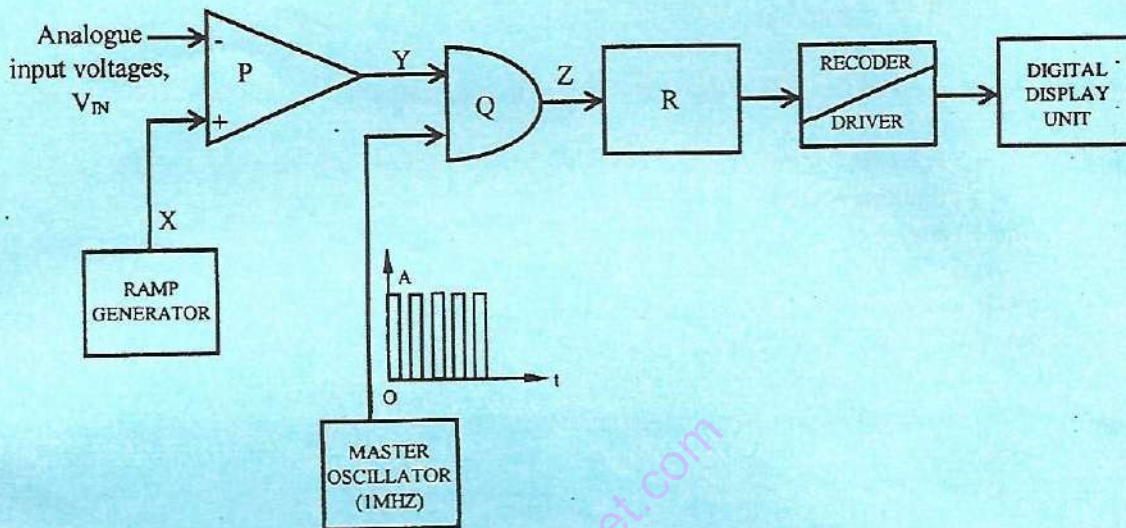


Fig. 2


- I. Identify the blocks marked P, Q and R.
 - II. Sketch the waveforms at points X, Y and Z. (11 marks)
- (b) Explain the function of each of the following in analogue indicating instruments:
- (i) controlling torque;
 - (ii) damping torque. (4 marks)
- (c) A voltmeter of resistance 100Ω reads 1.47 V when connected across a dry cell. A potentiometer is used to measure the e.m.f of the dry cell and balance is obtained at 73 cm with dry cell and 50 cm with a standard cell. The standard cell has an e.m.f of 1.018 V . Determine the:
- (i) e.m.f of the dry cell;
 - (ii) internal resistance of the dry cell. (5 marks)

4. (a) Define each of the following with respect to alternating current (a.c) generation:
- (i) form factor;
 - (ii) cycle;
 - (iii) waveform. (6 marks)
- (b) A rectangular coil has 40 runs and measures 30 cm by 20 cm. It is rotated at a speed of 1500 r.p.m in a uniform magnetic field of flux density 0.075 Wb/m^2 . The axis of rotation is at right angles to the direction of the flux. Determine the:
- (i) angular frequency, in rad/sec;
 - (ii) maximum value of flux;
 - (iii) maximum value of induced e.m.f. (8 marks)
- (c) A 3-phase star connected generator supplies a 3-phase balanced delta-connected load. The generator line voltage is 400 V.
- (i) Draw the circuit diagram for the connection.
 - (ii) Determine the phase voltage of the generator. (6 marks)
5. (a) A voltage, $v = 340 \sin \omega t$, is applied to a circuit and the resulting current is $i = 14 \sin(\omega t - 30^\circ)$. For the circuit, determine the:
- (i) impedance;
 - (ii) resistance;
 - (iii) reactance;
 - (iv) power;
 - (v) power factor. (10 marks)
- (b) A $15 \mu\text{F}$ capacitor is charged to 200 V through a $1.2 \text{ M}\Omega$ resistor. Determine the:
- (i) time constant;
 - (ii) initial charging current;
 - (iii) initial rate of rise of voltage across capacitor;
 - (iv) voltage across capacitor after 4.5 seconds from zero;
 - (v) time taken for the capacitor to be fully charged. (10 marks)

SECTION C: INSTRUMENTS AND ELECTRONIC FAULT DIAGNOSIS

Answer any *TWO* questions from this section.

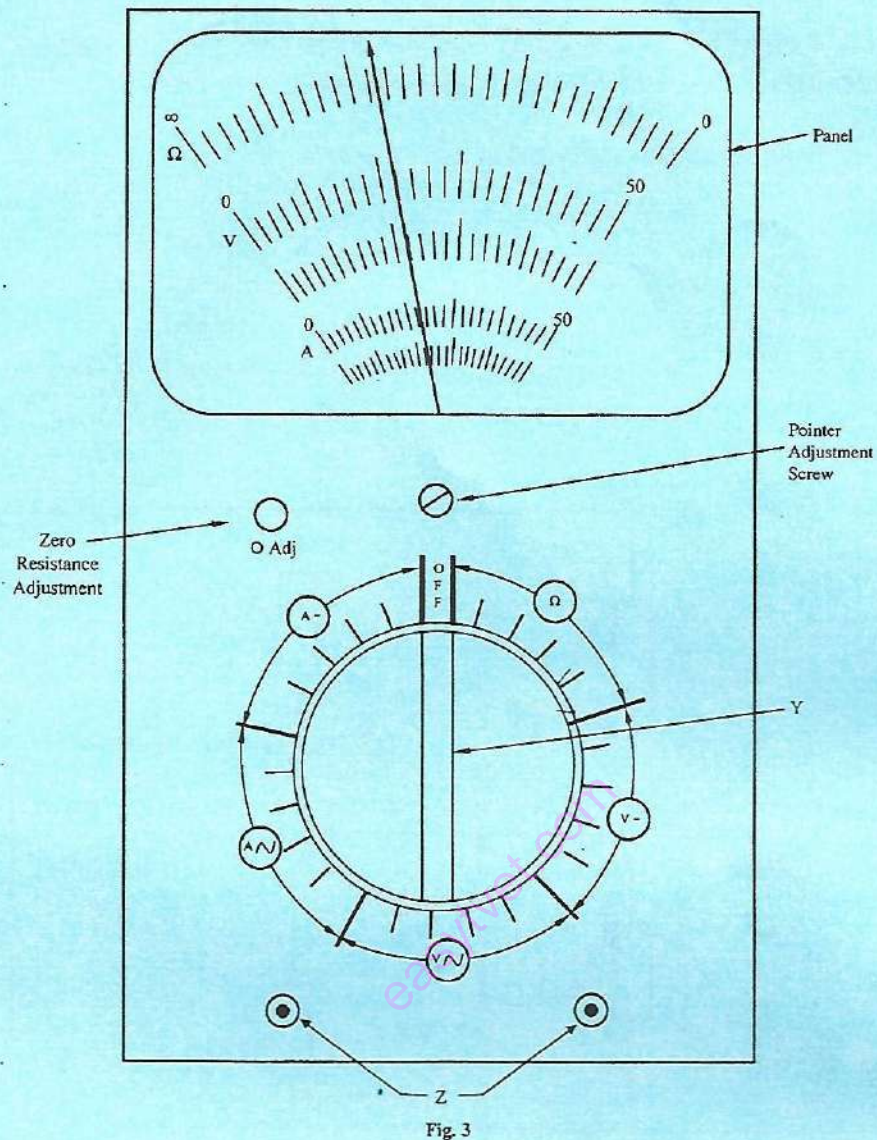6. (a) Define each of the following with respect to test signals:
- (i) amplitude;
 - (ii) rise time;
 - (iii) period. (6 marks)
- (b) (i) Sketch the waveform of a double sideband amplitude modulated wave, assuming sinusoidal modulation.
- (ii) The waveform in (b)(i) has a maximum value of 16 V and a minimum value of 4 V. Determine the depth of modulation. (6 marks)
- (c) A pulse waveform displayed on an oscilloscope has an amplitude of 15 V and a frequency of 6.25 KHz. The oscilloscope sensitivity settings are 10 V/cm and 20 μ s/cm. Determine the:
- (i) number of peak-to-peak cm occupied on the vertical axis;
 - (ii) period of the wave;
 - (iii) number of cm occupied by one cycle of the wave on the horizontal axis. (8 marks)
7. (a) Explain parallax error in measurements and state how it can be minimized. (3 marks)
- (b) **Figure 3** shows a diagram of the front panel of an analogue multimeter.
- (i) Identify and state the function of the parts labelled X, Y and Z.
 - (ii) State the meaning of the labels $V-$, $A \sim$ and Ω on the meter. (9 marks)



(c) Draw a labelled block diagram of a spectrum analyzer and describe its operation.

(8 marks)

8.

(a) (i) State **three** causes of premature failure in semiconductor devices.

(ii) State **three** precautions to take when testing digital integrated circuits.

(6 marks)

(b) Outline the procedure of testing a single-phase iron-cored transformer using an ohmmeter.

(5 marks)

(c) **Figure 4** shows a circuit diagram of a common-emitter transistor amplifier. The base emitter voltage $V_{be} = 0.7\text{ V}$ and the collector current $I_c = 3\text{ mA}$.

(i) Estimate the bias voltages at the test points:

TP₁

TP₂

TP₃

(ii) State the voltages at each test point when the resistor R_1 is open circuited.

(9 marks)

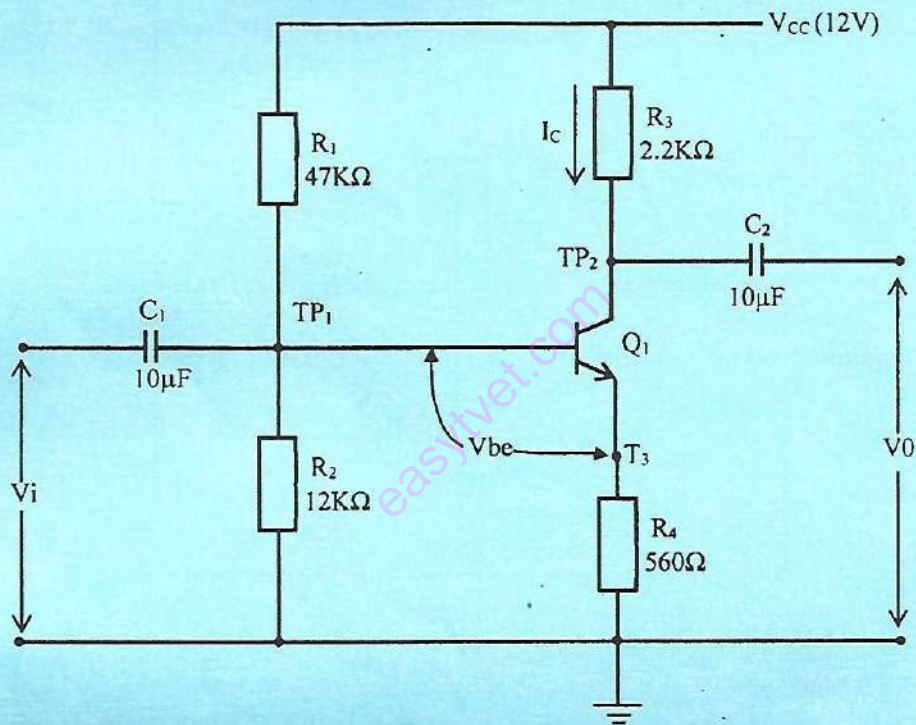


Fig. 4

Instruction set of

8080/8085

OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC
00	NOP	2B	DCX H	56	MOV D,M	81	ADD C	AC	XRA I	D7	RST 2
01	LXI B,D16	2C	INR L	57	MOV D,A	82	ADD D	AD	XRA L	D8	RC
02	STAX B	2D	DCR L	58	MOV E,B	83	ADD E	AE	XRA M	D9	-
03	INX B	2E	MVI L,D8	59	MOV E,C	84	ADD H	AF	XRA A	DA	JC Adr
04	INR B	2F	CMA	5A	MOV E,D	85	ADD L	B0	ORA B	DB	IN D8
05	DCR B	30	SIM	5B	MOV E,E	86	ADD M	B1	ORA C	DC	CC Adr
06	MVI B,D8	31	LXI SPD16	5C	MOV E,H	87	ADD A	B2	ORA D	DD	-
07	RLC	32	STA Adr	5D	MOV E,L	88	ADC B	B3	ORA E	DE	SBI D8
08	-	33	INX SP	5E	MOV E,M	89	ADC C	B4	ORA H	DF	RST 3
09	DAD B	34	INR M	5F	MOV E,A	8A	ADC D	B5	ORA L	E0	RPO
0A	LDAX B	35	DCR M	60	MOV H,B	8B	ADC E	B6	ORA M	E1	POP H
0B	DCX B	36	MVI M,D8	61	MOV H,C	8C	ADC H	B7	ORA A	E2	JPO Adr
0C	INR C	37	STC	62	MOV H,D	8D	ADC L	B8	CMP B	E3	XTHL
0D	DCR C	38	---	63	MOV H,E	8E	ADC M	B9	CMP C	E4	CPO Adr
0E	MVI C,D8	39	DAD SP	64	MOV H,H	8F	ADC A	BA	CMP D	E5	PUSH I
0F	RRC	3A	LDA Adr	65	MOV H,L	90	SUB B	BB	CMP E	E6	ANI D8
10	---	3B	DCX SP	66	MOV H,M	91	SUB C	BC	CMP I	E7	RST 4
11	LXI D,D16	3C	INR A	67	MOV H,A	92	SUB D	BD	CMP L	E8	RPE
12	STAX D	3D	DCR A	68	MOV L,B	93	SUB E	BE	CMP M	E9	PCHL
13	INX D	3E	MVI A,D8	69	MOV L,C	94	SUB H	BF	CMP A	EA	JPE Adr
14	INR D	3F	CMC	6A	MOV L,D	95	SUB L	C0	RNZ	EB	XCHG
15	DCR D	40	MOV B,B	6B	MOV L,E	96	SUB M	C1	POP B	EC	CPE Adr
16	MVI D,D8	41	MOV B,C	6C	MOV L,H	97	SUB A	C2	JNZ Adr	ED	---
17	RAL	42	MOV B,D	6D	MOV L,L	98	SBB B	C3	JMP Adr	EE	ERI D8
18	---	43	MOV B,E	6E	MOV L,M	99	SBB C	C4	CNZ Adr	EF	RST 5
19	DAD D	44	MOV B,H	6F	MOV L,A	9A	SBB D	C5	PUSH B	F0	RP
1A	LDAX D	45	MOV B,L	70	MOV M,B	9B	SBB E	C6	ADI D8	F1	POP PSW
1B	DCX D	46	MOV B,M	71	MOV M,C	9C	SBB H	C7	RST 0	F2	JP Adr
1C	INR E	47	MOV B,A	72	MOV M,D	9D	SBB L	C8	RZ	F3	DI
1D	DRC E	48	MOV C,B	73	MOV M,E	9E	SBB M	C9	RET Adr	F4	CP Adr
1E	MVI E,D8	49	MOV C,C	74	MOV M,H	9F	SBB A	CA	JZ	F5	PUSH PSW
1F	RAR	4A	MOV C,D	75	MOV M,L	A0	ANA B	CB	---	F6	ORI D8
20	RIM	4B	MOV C,E	76	HLT	A1	ANA C	CC	CZ Adr	F7	RST 6
21	LXI H,D16	4C	MOV C,H	77	MOV M,A	A2	ANA D	CD	CALL Adr	F8	RM
22	SHLD Adr	4D	MOV C,L	78	MOV M,B	A3	ANA E	CE	ACI D8	F9	SPHL
23	INX H	4E	MOV C,M	79	MOV M,C	A4	ANA H	CF	RST 1	FA	JM Adr
24	INR H	4F	MOV C,A	7A	MOV M,D	A5	ANA L	D0	RNC	FB	E1
25	DCR H	50	MOV D,B	7B	MOV M,E	A6	ANA M	D1	POP D	FC	CM Adr
26	MVI H,D8	51	MOV D,C	7C	MOV M,H	A7	ANA A	D2	JNC Adr	FD	---
27	DAA	52	MOV D,D	7D	MOV M,L	A8	XRA B	D3	OUT D8	FE	CPI D8
28	---	53	MOV D,E	7E	MOV M,M	A9	XRA C	D4	CNC Adr	FF	RST 7
29	DAD H	54	MOV D,H	7F	MOV M,A	AA	XRA D	D5	PUSH D		
2A	LHLD Adr	55	MOV D,L	80	ADD B	AB	XRA E	D6	SUI D8		

D8 = constant, or logical/arithmetic expression that evaluates to an 8-bit data quantity. D16 = constant, or logical/arithmetic expression that evaluates to a 16-bit data quantity. Adr = 16-bit address.

THIS IS THE LAST PRINTED PAGE.

1522/204

9

Turn over

1602/204

June/July 2023