

061006T4ICT

ICT LEVEL 6

IT/OS/ICT/CC/1/6

APPLY BASIC ELECTRONICS

Nov. /Dec. 2022



THE KENYA NATIONAL EXAMINATIONS COUNCIL

WRITTEN ASSESSMENT

Time: 3 hours

INSTRUCTIONS TO CANDIDATE

Maximum marks for each question are indicated in brackets ().

*This paper consists of **TWO** sections: A and B.*

Answer questions as per instructions in each section.

You are provided with a separate answer booklet.

*This paper consists of **THREE (3)** printed pages*

Candidates should check the question paper to ascertain that all pages are printed as

Indicated and that no questions are missing

SECTION A (40 MARKS)

Answer ALL questions in this section.

1. Define an electronic circuit. (2 marks)
2. Describe any **FOUR** components found in an electronic circuit. (4 marks)
3. Briefly describe any **FOUR** types of electrical circuits (4 marks)
4. Distinguish between a loop network and a mesh network of an electric circuit. (4 marks)
5. Define electrical resistance. (2 marks)
6. Outline any **TWO** application areas of holographic memory in a computer. (4 marks)
7. List any **FOUR** types of capacitors. (4marks)
8. Differentiate between an atom and atomic structure. (2 marks)
9. Describe the structure of a matter (4 marks)
10. Name any **TWO** types of semi-conductor materials used. (2 marks)
11. Distinguish between P-Type materials and N-Type materials giving examples in each one of them. (4 marks)
12. Using an example illustrate why a PN Junction is used. (4 marks)

SECTION B: (60 MARKS)

Answer any THREE questions in this section

13. (a) Explain how valence electrons determine the electrical properties of a material (6 Marks)
- (b) Describe the valence band, conduction band and forbidden energy gap with the help of energy level diagram. (6 Marks)
- (c) List three important properties of semiconductors. (6 marks)
- (d) Define a semi-conductor in terms of resistivity? (2 Marks)
14. (a) Explain the formation of a depletion Layer in a *pn* junction (10 Marks)
- (b) Discuss the behavior of a *pn* junction under forward biasing. (6 Marks)
- (c) Define the following terms:
- i. Breakdown voltage (2 Marks)
 - ii. Knee voltage (2 Marks)
15. (a) Explain the operation of transistor as an amplifier. (10 Marks)
- (b) Name the three possible transistor connections. (6 Marks)
- (c) In a transistor, $\beta = 45$, the voltage across $5k\Omega$ resistance which is connected in the collector circuit is 5 volts. Find the base current for the common emitter connection. (4 Marks)
16. a) With aid of a sketch, outline the configurations of PN junction diode showing both the input signal and output (8 Marks)
- b) Discuss any six challenges of emerging trends in electronic manufacturing. (12 Marks)