1601/105 1602/105 ELECTRICAL AND SOLAR INSTALLATION TECHNOLOGY June/July 2021 Time: 3 hours



## THE KENYA NATIONAL EXAMINATIONS COUNCIL

# CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONICS ENGINEERING (POWER OPTION) (TELECOMMUNICATION OPTION)

#### **MODULE I**

ELECTRICAL AND SOLAR INSTALLATION TECHNOLOGY

3 hours

#### INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Non-programmable scientific calculator/mathematical tables;

Answer booklet;

Drawing instruments.

This paper consists of TWO sections; A and B.

Answer any THREE questions from section A and any TWO questions from section B in the answer booklet provided.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 6 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

# SECTION A: ELECTRICAL INSTALLATION TECHNOLOGY

Answer any THREE questions from this section.

1.	(a)	(i)	(i) State three IEE regulations requirement for the consumers intake point.		
		(ii)	Draw a line diagram showing the sequence of control equipment at a consumer's intake point.	he	
				(8 marks)	
	(b)	(i)	State two ways of controlling a lamp from multiple positions.		
	0	(ii) Using the ceiling rose method, draw a wiring diagram of one lamp controlled from one position.			
				(5 marks)	
	(0)	Outl	ine three IEE regulation requirements regarding 13 A socket outlets.	(3 marks)	
	(d)	Drav	v and label a diagram of a non-instantaneous water heating system.	(3 marks)	
			a dagram of a non-instantaneous water heating system.	(4 marks)	
2.	(a)	Nam	e three:		
b)		(i)	authorities of power generation in Kenya.		
		(ii)	sources of electrical energy		
				(6 marks)	
	(b)	Draw	a labelled block diagram of a diesel power plant.	(4 marks)	
	(E)	Describe each of the following parts of a hydro electric power plant.			
		(i) (ii)	dam; generator.		
		(**)	generator.	(Amarday)	
	(d)	Draw	the following electrical distribution system:	(4 marks)	
		(i)	A.C two wire;		
		(ii)	A.C three phase 3 wire.		
				(6 marks)	

- 3. **(a)** State three properties of a good: (i) conductor; (ii) insulator. (6 marks) Describe the construction of a P.V.C cable. (b) (2 marks) (13) Outline the procedure of soldering a cable joint using a soldering iron. (c) (4 marks) (d) State three IEE regulation requirements regarding cables and conductors. (i) Figure 1 show the construction diagram of a PILCSWA cable. (ii) Load Lover Binter Fig. 1 Name the parts labelled A, B, C, D and E. (8 marks) State two reasons of using protective devices in electrical circuits. (a) (2 marks) (b) Explain the following as used in electrical circuit protection: (i) circuit breaker; (ii) short circuit. (4 marks) (c) (H) State two advantages and two disadvantages of rewirable fuses;
  - (ii) Draw a labelled diagram of a catridge fuse;
    - (II) List three colour codes and their ratings for the fuse in c(ii)(I).
  - (d) Illustrate the parts of an earthing system. (4 marks)

(10 marks)

- Describe each of the following parts of a D.C machine: 5. (a) (i) Brushes; (ii) Armature: (iii) Commutator. (6 marks) (b) Distinguish between a cummulative compound and a differential compound (i) wound generator. Draw the equivalent circuit diagrams of each of the following D.C machines: (ii) shunt motor; 3 (II) · separately excited generator. (6 marks) (c) Figure 2 shows a diagram of a single phase A.C induction motor: unding 76 AC Supply Fig. 2 (i) Identify the type of motor. Name the parts labelled A, B, C, D and E. (ii) Explain the function of the part labelled B. (iii) (8 marks) COLOR
  - COLOR FUSE RATING
    GVEEN 43 A
    RED 30 A
    VELLOW 20 A
    BLUE 15 A
    1602/105

1601/105 June/July 2021

### SECTION B: SOLAR INSTALLATION TECHNOLOGY

Answer any TWO questions from this section.

- Explain the following as used in solar electric systems: (a) 6.
  - (i) photo voltaic effect;
  - (ii) photo electric effect.

(4 marks)

Draw and label a diagram showing the construction of a solar cell. (b)

(5 marks)

- (c) Explain the functions of the following accessories:
  - socket outlets; (i)
  - (ii) ceiling roses.

(4 marks)

- Name three wiring systems used in P.V solar installations; Shoat's (d) W
  - Illustrate how the polarity test is carried out on a lighting circuit. (ii)

(7 marks)

- (7.)Define each of the following solar energy terminologies: (a)
  - (i) Insolation;
  - (ii) Direct radiation. Heat from the son that venetics early the Bath when the day Draw a labelled diagram of a solar flat plate collector. (4 marks)
  - (b)

(6 marks)

(c) State four merits of solar water heater.

(4 marks)

With aid of a labelled diagram, explain the green house effect. (d)

(6 marks)

- 8. Explain each of the following as used in designing solar electrical installations: (a)
  - (i) sizing;
  - (iii) daily load energy demand.

(4 marks)

(b) Explain the factors considered when selecting the size of each of the following P.V solar devices: (i) inverter; (iii) charge controller. (4 marks) (c) A house has the following solar electric installation requirements: Four - 8 W lamps operated for 3 hours daily 1 transistor radio rated 10 W operated 3 hours daily 1 mobile charger rated 4 W operated 2 hours daily. Determine the (i) total daily energy demand; (ii) total daily energy requirements if the losses are 15% of the load. (7 marks) (d) Outline the: maintenance procedure for lamps and switches in a solar installation; (i) three precautions to be observed in a battery charging room. (ii) (5 marks)

THIS IS THE LAST PRINTED PAGE.